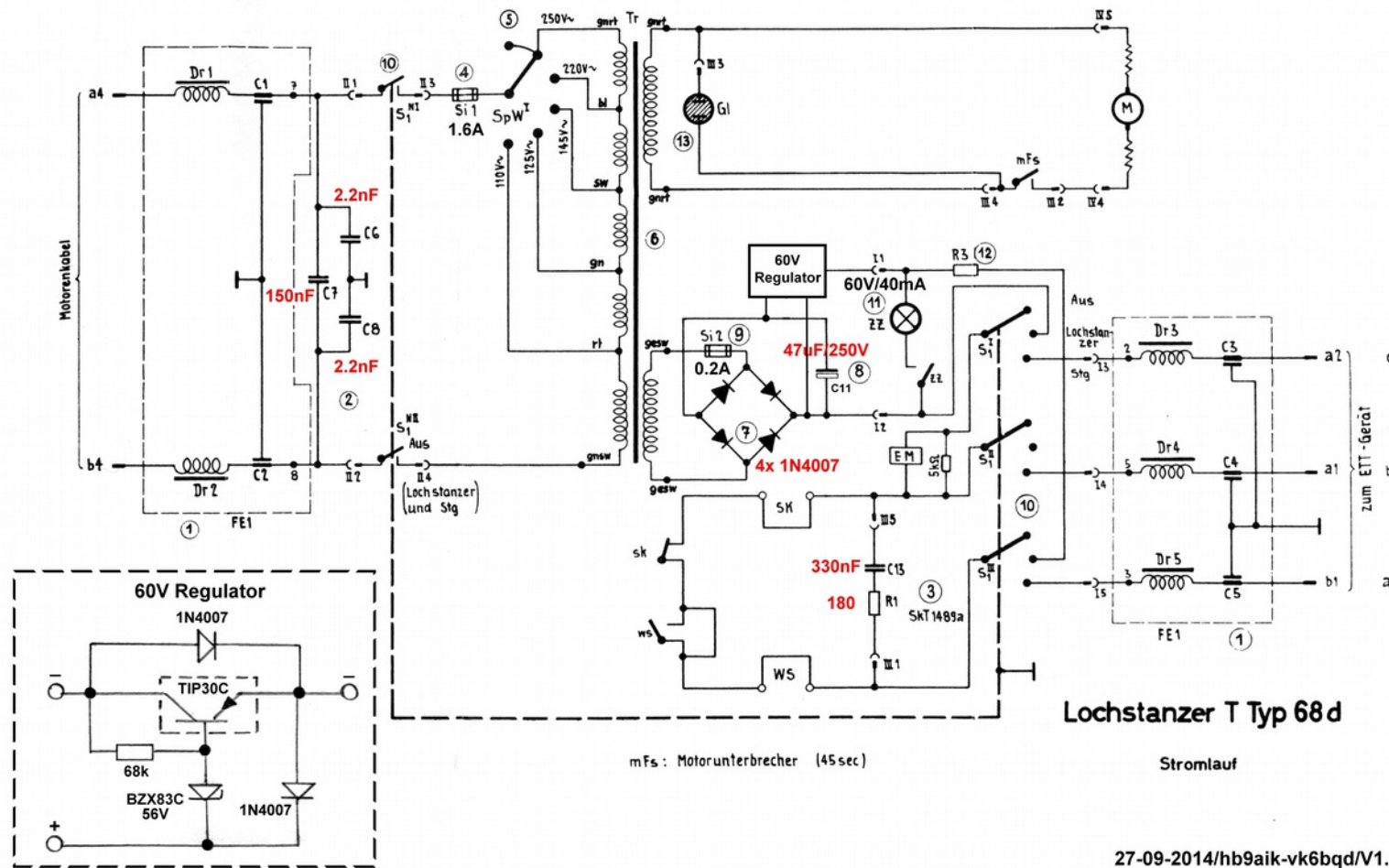


The power supply between the EMC filter and the bottom plate in this Swiss version provides line current for local punching operations (and the end-of-line lamp). The machine was often used to prepare punched tapes for later transmission on other systems.

T68d (CH) Internal Power Supply



Corrosion on capacitors and solder lugs required a new strip, some rewiring and new capacitors. Silicon diodes replace the selenium rectifier. The resulting high voltage is regulated to 60V mainly to protect the end-of-line lamp (11).